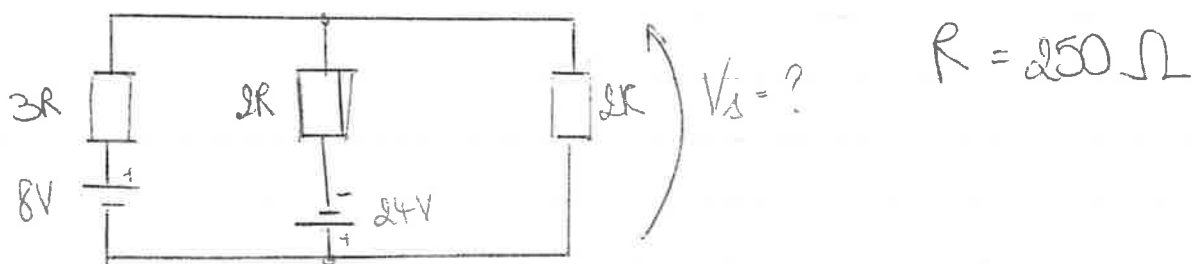


Übungen Prof. Dr. Stuk 3

Üb 1



① parallelschaltung $3R \parallel 2R$

$$\frac{1}{R_{\text{tot}}} = \frac{1}{2R} + \frac{1}{3R} = \frac{5}{6R}$$

$$\Rightarrow R_{\text{tot}} = \frac{6}{5}R$$


② ~~parallelschalt.~~ $\frac{6}{5}R \parallel 2R$ Spannungsteiler

$$V_1 = \frac{6/5R}{2R + 6/5R} \cdot 24V = -9V$$

③ parallel $2R \parallel 2R$
 $R_{\text{tot}} = R$

④ Spannungsteiler: $V_1 = \frac{R}{4R} \cdot 8V = 2V$


$$\Rightarrow V_1 = -9V + 2V = -7V$$

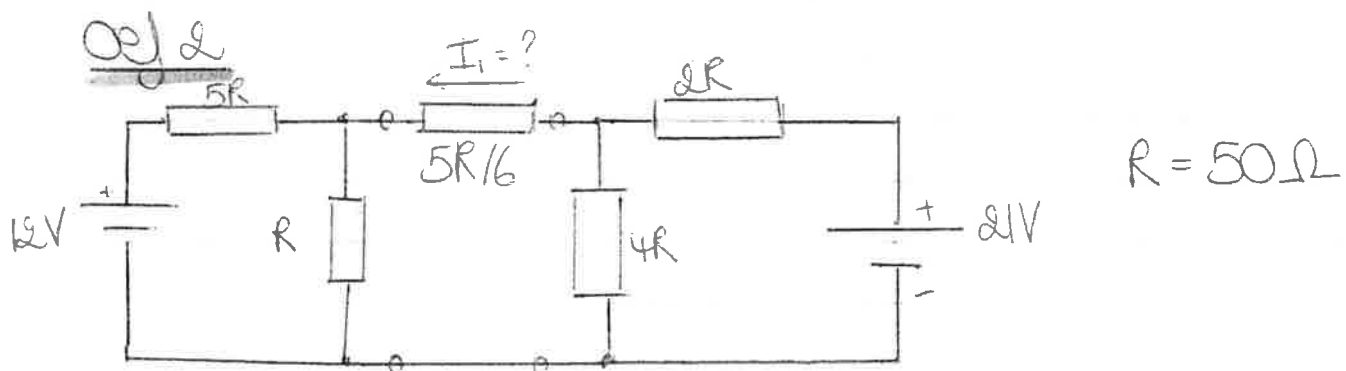

① Thévenin-equivalent

$$1/R_T = \frac{1}{5R} + \frac{1}{R} = \frac{6}{5R} \Rightarrow R_T = \frac{5}{6}R$$


$$V_T = \frac{R}{6R} \cdot 12V = 2V$$

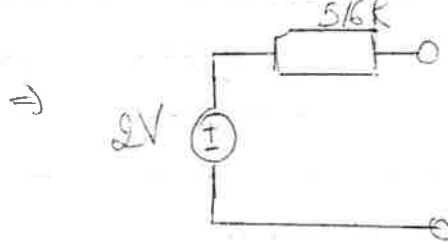

② Thévenin-equivalent

$$1/R_T = \frac{1}{4R} + \frac{1}{2R} = \frac{3}{4R} \Rightarrow R_T = \frac{4}{3}R$$

$$V_T = \frac{4R}{6R} \cdot 21V = 14V$$

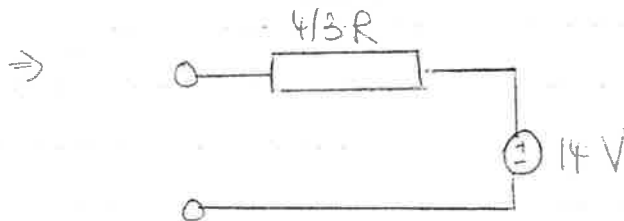

③ Serieschaltung: $R = \frac{5}{6}R + \frac{4}{3}R + \frac{5}{6}R = 3R$


④ Superposition:

$$+ I = \frac{V}{R} = \frac{14V}{150\Omega} = 9 \cdot 10^{-2}$$

$$+ I = \frac{-2V}{150\Omega} = -0,013$$

$$\Rightarrow I = 0,08 = 80 \text{ mA}$$

oef 3

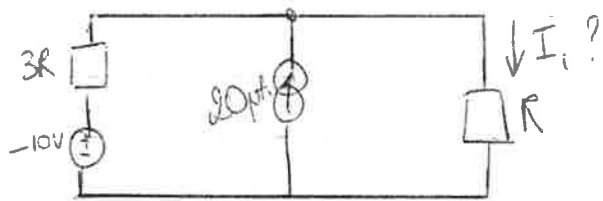

$$R = 500 \text{ k}\Omega$$

① ~~Thévenin-equivalent~~
 ~~$R_T = 3R$~~

① Strombron = open keten
 + Serie $R = 4R$


$$I = \frac{V}{R} = \frac{-10V}{4R} = \frac{-10V}{2000 \text{ k}\Omega} = -5 \text{ nA}$$

② Spanningsbron = kortsluiting
 + stroombron:

$$I_1 = \frac{3R}{4R} \cdot 20 \text{ pA} = 15 \text{ pA}$$

$$③ I_1 = -5 \text{ nA} + 15 \text{ nA} = 10 \text{ nA}$$

oef 4

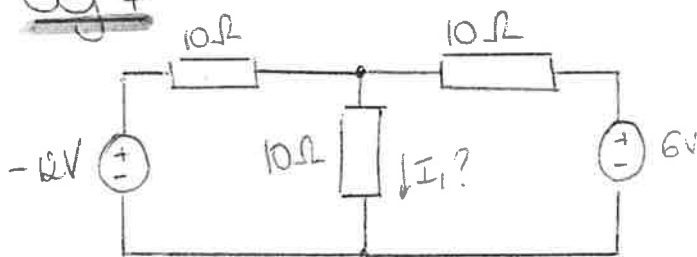

→ superpositie

① parallel: $1/R_T = 1/10 + 1/10 = 2/10 \Rightarrow R_T = 5 \Omega$

→ Spannungsdeler: $V_1 = \frac{5 \Omega}{15 \Omega} \cdot -2V = -4V$


② Parallel: $1/R_T = 2/10 \Rightarrow R_T = 5 \Omega$

→ $V_1 = \frac{5 \Omega}{15 \Omega} \cdot 6V = 2V$

$$\Rightarrow V_1 = -4V + 2V = -2V$$

$$I = \frac{V}{R} = \frac{-2V}{10\Omega} = -0,2A = -200mA$$

ex 5

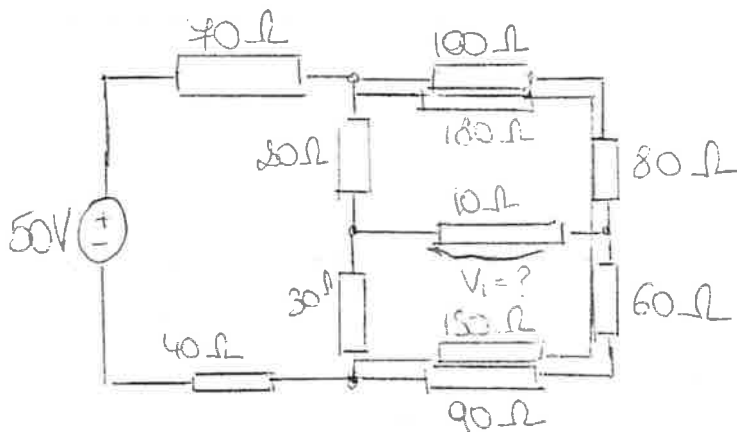

① 2 x serie : $R_1 = 100\Omega + 80\Omega = 180\Omega$
 $R_2 = 90\Omega + 60\Omega = 150\Omega$

② parallel : $\frac{1}{R_3} = \frac{1}{30} + \frac{1}{150} = \frac{1}{25} \Rightarrow R_3 = 25\Omega$

$$\frac{1}{R_4} = \frac{1}{20} + \frac{1}{180} = \frac{1}{18} \Rightarrow R_4 = 18\Omega$$

$$\frac{1}{R_5} = \frac{1}{40} + \frac{1}{25} = \frac{13}{200} \Rightarrow R_5 = 200/13\Omega$$

$$\frac{1}{R_6} = \frac{1}{18} + \frac{1}{70} = \frac{22}{315} \Rightarrow R_6 = 315/22\Omega$$

$$\frac{1}{R_7} = \frac{13}{200} + \frac{22}{315} \Rightarrow R_7 =$$

Def 6

$$+ 1/R_T =$$

$$+ \text{Serie} : R_{\text{tot}} = 50 + 50 = 100$$

$$+ \text{Thévenin} : 1/R_T = \frac{1}{100} + \frac{1}{100} \Rightarrow R_T = 50$$

$$V_T = \frac{100}{200} \cdot 20 = 10 \text{ V}$$

$$+ \text{Serie} : R_{\text{tot}} = 50 + 25 + 25 = 100$$

Def 8

$$+ \text{Thévenin} : 1/R_T = \frac{1}{30} + \frac{1}{30} = \frac{2}{30} \Rightarrow R_T = 15 \Omega$$

$$V_T = \frac{30}{60} \cdot 48 \text{ V} = 24 \text{ V}$$

$$+ \text{Serie} : R_{\text{tot}} = 15 \Omega + 15 \Omega = 30 \Omega$$

$$+ \text{Thévenin} : 1/R_T = \frac{1}{30} + \frac{1}{30} \Rightarrow R_T = 15 \Omega$$

$$V_T = \frac{30}{60} \cdot 24 \text{ V} = 12 \text{ V}$$

$$+ \text{Serie} : R_{\text{tot}} = 15 \Omega + 15 \Omega = 30 \Omega$$

$$+ \text{Thévenin} : 1/R_T = \frac{1}{30} + \frac{1}{30} \Rightarrow R_T = 15 \Omega$$

$$V_T = 6 \text{ V}$$

$$+ \text{Serie} : R_{\text{tot}} = 30 \Omega$$

$$+ \text{Thévenin} : 1/R_T = \frac{1}{30} + \frac{1}{15} \Rightarrow R_T = 10 \Omega$$

$$V_T = \frac{15}{45} \cdot 6 \text{ V} = 2 \text{ V}$$

ex 8

$$\frac{1}{R_1} = \frac{2}{15} \Rightarrow R_1 = \frac{15}{2}$$

$$\frac{1}{R_2} = \frac{2}{15} + \frac{1}{30} = \frac{5}{30} \Rightarrow R_2 = 6$$

$$\frac{1}{R_3} = \frac{1}{15} + \frac{1}{6} = \frac{4}{30} \Rightarrow R_3 = \frac{30}{4}$$

$$\frac{1}{R_4} = \frac{4}{30} + \frac{1}{30} = \frac{5}{30} \Rightarrow R_4 = \frac{30}{5} = \frac{15}{4}$$

$$\frac{1}{R_5} = \frac{1}{15} + \frac{4}{15} = \frac{5}{15} \Rightarrow R_5 = 3$$

$$\frac{1}{R_6} = \frac{1}{30} + \frac{1}{3} \Rightarrow R_6 = \frac{30}{11}$$

$$\frac{1}{R_7} = \frac{1}{30} + \frac{11}{30} \Rightarrow R_7 = \frac{30}{12} = \frac{15}{6} = \frac{5}{2}$$

Oefeningen hoofdstuk 4

oef 1

1) + Knoopwet: $-i_{R_2} + I_A - i_L = 0$
 $\Rightarrow i_{R_1} = I_A - i_L$

divuwt: $R_1 i_{R_1} + R_2 i_{R_2} - V_L = 0$

formule span: $V_L(t) = L \cdot \frac{di_L(t)}{dt}$

$$\Leftrightarrow R_1 I_A - R_1 i_L - R_2 i_{R_2} - L \frac{di_L(t)}{dt} = 0$$

$$R_2 I_A = (R_1 + R_2) i_L + L \frac{di_L(t)}{dt} \quad (L \text{ DVCC})$$

① K.V.: $L \cdot \lambda + R_1 + R_2 = 0$

$$\lambda = -\frac{(R_1 + R_2)}{L} = -\frac{1}{\tau} \quad \text{met } \tau = \frac{L}{R_1 + R_2}$$

A.O.: $i_L = B \cdot e^{-t/\tau}$

② $e(t) = \frac{R_2 I_A}{R_1 + R_2}$

③ A.O.: $i_L = B \cdot e^{-t/\tau} + \frac{R_1 I_A}{R_1 + R_2}$

④ B? $i_L(0) = 0 \Rightarrow 0 = B + \frac{R_1 I_A}{R_1 + R_2}$

$$B = -\frac{R_1 I_A}{R_1 + R_2} = -0,01 = -10 \text{ mA}$$

$$i_L(t) = -10 \text{ mA} \cdot e^{-t/\tau} + 10 \text{ mA} \\ = 10 \text{ mA} (1 - e^{-t/\tau})$$

$$\begin{aligned}
 2) \quad v_L(t) &= L \cdot \frac{di_L(t)}{dt} = -L \cdot \frac{R_1 I_A}{R_1 + R_2} \cdot \left(-\frac{1}{\tau}\right) \cdot e^{-t/\tau} \\
 &= +L \cdot \frac{R_1 I_A}{R_1 + R_2} \cdot \frac{R_1 + R_2}{L} \cdot e^{-t/\tau} \\
 &= 20V \cdot e^{-t/2}
 \end{aligned}$$

$$\begin{aligned}
 3) \quad t_1 &= 1 \mu s \cdot \ln(2) \\
 \Rightarrow \frac{t_1}{1 \mu s} &= -\ln 2 \\
 e^{-t_1/\tau} &= e^{-\ln 2} = \frac{1}{2}
 \end{aligned}$$

$$\begin{aligned}
 i_L(t) &= 10 \text{ mA} \left(1 - \frac{1}{2}\right) = 5 \text{ mA} \\
 v_L(t) &= 10V
 \end{aligned}$$

Def 2

$$\begin{aligned}
 1) \quad v_2(t) \quad \text{Knoten: } & \cancel{V_A - V_{C1} - V_{C2} = 0} \quad \text{Knoten: } V_A - V_{R1} - V_2 = 0 \\
 & \cancel{V_A = V_{C1} + V_{C2}} \quad \begin{aligned} & V_{R1} = V_A - V_2 \\ & V_2 = V_{R2} \\ & V_A - V_{R1} - V_2 = 0 \\ & \underline{V_2 = V_A - V_2} \end{aligned} \\
 & + V_{C1} = R
 \end{aligned}$$

$$\begin{aligned}
 \text{Knoten: } & i_{R1} + i_{C1} = i_{R2} + i_{C2} \\
 & \frac{V_{R1}}{R_1} + C_1 \frac{dV_{C1}}{dt} = \frac{V_{R2}}{R_2} + C_2 \frac{dV_{C2}}{dt} \\
 R_1 = R_2 \quad \downarrow & \\
 \text{Knoten: } & \frac{1}{R} (V_{R1} - V_{R2}) = C_1 \left(\frac{dV_2}{dt} - \frac{dV_{C1}}{dt} \right) \\
 & \downarrow \frac{1}{R} (V_A - 2V_2) = C \left(\frac{dV_2}{dt} - \frac{d(V_A - V_2)}{dt} \right)
 \end{aligned}$$

oef 3

$$\begin{aligned} a) \quad V_A &= V_C + R_1 \cdot I_1 \\ &= V_C + R_1 \cdot C \cdot \frac{dV_C(t)}{dt} \end{aligned}$$

$$\textcircled{1} \text{ K.V. : } 1 + R_1 \cdot C \cdot \lambda = 0$$

$$\lambda = -\frac{1}{R_1 C} = -\frac{1}{\tau} \quad \text{met } \tau = R_1 \cdot C = 120 \mu\text{s}$$

$$\textcircled{2} \text{ A.O. : } V_C(t) = B \cdot e^{-t/\tau}$$

$$\textcircled{3} e(t) = \frac{V_A}{1} = 20 \text{ V}$$

$$\textcircled{4} \text{ A.O. : } V_C(t) = B \cdot e^{-t/\tau} + 20 \text{ V}$$

$$\textcircled{5} \text{ Beginvormwaarden : } V_C(0) = B + 20 \text{ V} = 0 \Rightarrow B = -20 \text{ V}$$

$$V_C(t) = -20 \text{ V} \cdot e^{-t/\tau} + 20 \text{ V} = 20 \text{ V} (1 - e^{-t/\tau})$$

$$V_C(t_1) = 10 \text{ V} \quad \text{en } 2$$

$$\frac{t_1}{120} = \ln 2$$

$$\Rightarrow e^{-t_1/\tau} = \frac{1}{2} \Rightarrow V_C(t_1) = 20 \text{ V} \left(1 - \frac{1}{2}\right) = 10 \text{ V}$$

$$\begin{aligned} b) \quad V_A &= V_C + R_1 \cdot I_1 + R_1 \cdot I_2 \\ &= V_C + R_1 \cdot C \cdot \frac{dV_C(t)}{dt} + \frac{V_C}{R_2} \cdot R_1 = V_C \cdot \frac{R_2 + R_1}{R_2} + R_1 C \frac{dV_C}{dt} \end{aligned}$$

$$\textcircled{1} \text{ K.V. : } \frac{R_2 + R_1}{R_2} + R_1 C \lambda = 0$$

$$\Rightarrow \lambda = -\frac{(R_2 + R_1)}{R_2 R_1 C} = -\frac{1}{\tau} \quad \text{met } \tau = \frac{R_2 R_1 C}{R_2 + R_1} = 30 \mu\text{s}$$

$$\text{A.O. : } V_C(t) = A \cdot e^{-t/\tau}$$

$$\textcircled{2} e(t) = V_A \cdot \frac{R_2}{R_1 + R_2} = 5V$$

$$\text{A.O.} \quad A \cdot e^{-\frac{(t-t_1)}{\tau}} + 5V = v_C(t)$$

$$\textcircled{3} \text{Beginwaarden: } 0 = A \cdot e^{-\frac{(t_0+t_1)}{\tau}} + 5V \Rightarrow A = +5V$$

$$\Rightarrow v_C(t) = 5V(1 + e^{-t/\tau})$$

$$\frac{-t_2}{30 \mu s} = 5 \cdot \ln 2$$

$$e^{-\frac{(t+t_1)}{50}} = \frac{1}{2}$$

$$= 5V \left(1 + \frac{1}{2}\right) = 7,5V$$

oef 4

$$a) \text{ Knoopwet: } I_A - i_{R_1} - i_L - i_{R_2} = 0$$

$$i_{R_1} = I_A - i_L - i_{R_2}$$

$$\text{Luswet: } R_1 i_{R_1} - V_L = 0$$

$$R_1 (I_A - i_L - i_{R_2}) - L \cdot \frac{di_L(t)}{dt} = 0$$

$$R_1 I_A - R_1 i_L - i_{R_2} R_1 - L \cdot \frac{di_L(t)}{dt} = 0$$

$$R_1 I_A = L \cdot \frac{di_L(t)}{dt} + R_1 i_L + V_L$$

$$= 2L \frac{di_L(t)}{dt} + R_1 i_L$$

$$\textcircled{1} \text{ K.V.: } 2L\lambda + R_1 = 0$$

$$\lambda = -\frac{R_1}{2L} = -\frac{1}{\tau} \text{ met } \tau = \frac{2L}{R_1} = 40 \text{ ns}$$

$$\text{A.O.} \quad A \cdot e^{-t/\tau} = i_L(t)$$

$$\textcircled{2} \quad e(t) = \frac{R_1 I_A}{R_1} = I_A = 40 \text{ mA}$$

$$\text{A.O.: } i_L(t) = A \cdot e^{-t/\tau} + 40 \text{ mA}$$

$$\textcircled{3} \quad \text{B.V.: } i_L(0) = A + 40 \text{ mA} = 0 \\ \Rightarrow A = -40 \text{ mA}$$

$$\text{A.O.: } i_L(t) = 40 \text{ mA} (1 - e^{-t/\tau})$$

$$t_1 = 80 \text{ ns. En 2}$$

$$\frac{t_1}{40 \text{ ns}} = 2. \text{ En 2}$$

$$e^{-\frac{t_1}{\tau}} = \frac{1}{4}$$

$$i_L(t_1) = 40 \text{ mA} \left(1 - \frac{1}{4}\right) = 30 \text{ mA}$$

$$\text{b) } L \cdot \frac{di_L(t)}{dt} = -R_L \cdot i_L \quad (\text{2 aparte kring})$$

$$L \cdot \frac{di_L(t)}{dt} + R_L \cdot i_L = 0$$

$$\textcircled{1} \quad \text{K.V.: } L \cdot \lambda + R_L = 0$$

$$\lambda = -\frac{R_L}{L} = -\frac{1}{\tau_2} \quad \text{met } \tau_2 = \frac{L}{R_L} = 80 \text{ ns}$$

$$\text{A.O.: } i_L(t) = A \cdot e^{-\frac{(t-t_1)}{\tau_2}}$$

$$\textcircled{2} \quad e(t) = 0$$

$$\textcircled{3} \quad \text{B.V.: } i_L(t_1) = 30 \text{ mA} = A \\ i_L(t) = 30 \text{ mA} \cdot e^{-\frac{(t-t_1)}{\tau_2}}$$

entra af



$$+ \text{Knooppunt: } I_{e1} + I_A + I_B + I_L + \frac{V_{ce}}{R_e} = 0 \Rightarrow I_{e1} = -I_A + I_B - I_L - \frac{V_{ce}}{R_e}$$

$$\text{luswet: } R_1 I_{e1} - V_L = 0$$

$$R_1 I_B - R_1 I_A - V_L - R_1 \frac{V_{ce}}{R_e} - V_L = 0$$


oefeningen #5

oef 1

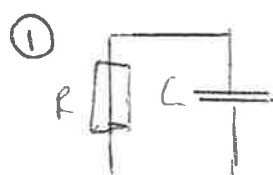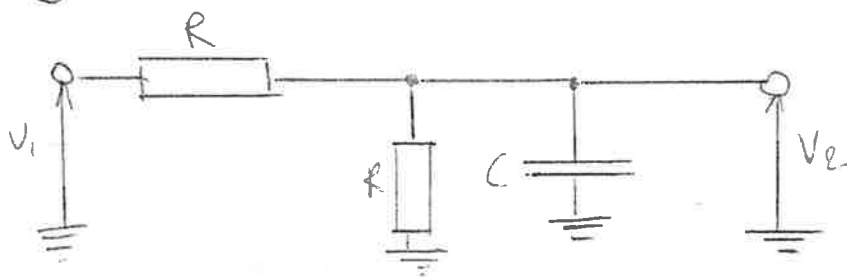

→ parallel
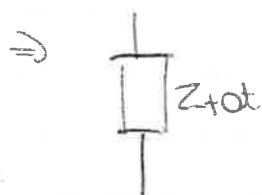
$$Z_C = \frac{1}{j\omega C} = \frac{1}{pC} \quad \text{met } p = j\omega$$



$$\frac{1}{Z_{tot}} = \frac{1}{R} + pC = \frac{1 + R p C}{R}$$
$$\Rightarrow Z_{tot} = \frac{R}{1 + R p C}$$

② Spanningsdeler:

$$V_2 = \frac{Z_{tot}}{R + Z_{tot}} \cdot V_1$$

$$\frac{V_2}{V_1} = \frac{\frac{R}{1 + R p C}}{R + \frac{R}{1 + R p C}} = \frac{1}{1 + R p C}$$

$$= \frac{1}{1 + R p C}$$
$$= \frac{1}{2} \cdot \frac{1}{1 + \frac{R p C}{2}}$$

$$p = j\omega = j 2\pi f$$

$$= \frac{1}{2} \cdot \frac{1}{1 + R C j\pi f}$$

$$= \frac{1}{2} \cdot \frac{1}{1 + j \frac{f}{f_c}} \quad \text{met } f_c = \frac{1}{R C} = 600 \text{ Hz}$$


③ Amplitude transfer

$$\left| \frac{V_2}{V_1} \right| = \frac{1}{2} \cdot \frac{1}{\sqrt{1 + \left(\frac{f}{f_c} \right)^2}}$$


wann $f \ll f_c$: $\left| \frac{V_2}{V_1} \right| \approx \frac{1}{2} \Rightarrow \#dB = 20 \log \frac{1}{2} = -6dB$

$f = f_c$: $\left| \frac{V_2}{V_1} \right| = \frac{1}{2\sqrt{2}} \Rightarrow \#dB = 20 \log \left(\frac{1}{2\sqrt{2}} \right) = -9dB$

$f \gg f_c$: $\left| \frac{V_2}{V_1} \right| \approx \frac{1}{2} \cdot \frac{f_c}{f} \Rightarrow \#dB = 20 \log f_c - 20 \log f + 20 \log \left(\frac{1}{2} \right)$

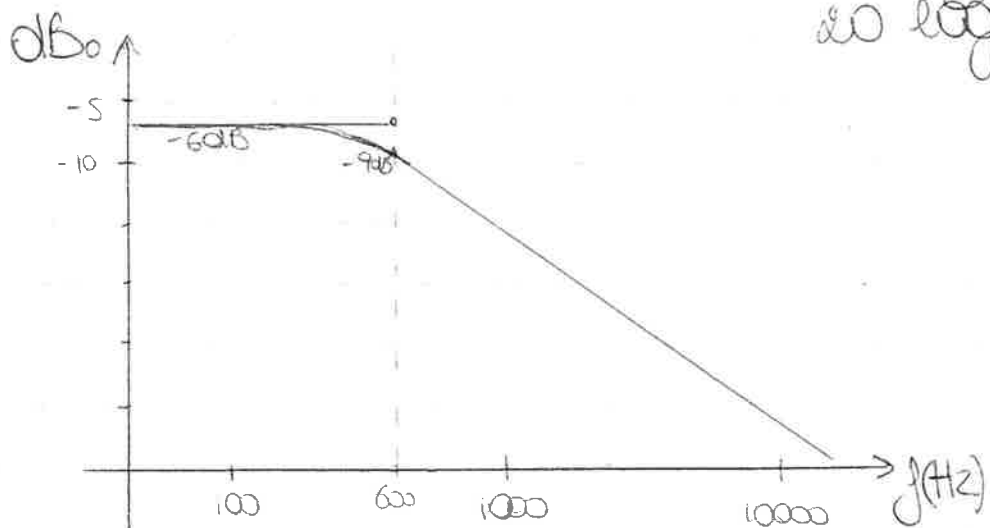

oef 2

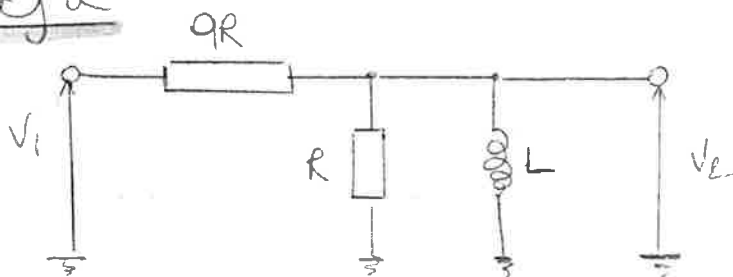

① $Z_L = j\omega L$ & $Z_R = R$ & parallel

$$\Rightarrow \frac{1}{Z_{tot}} = \frac{1}{R} + \frac{1}{j\omega L} = \frac{R + j\omega L}{Rj\omega L}$$

$$\Rightarrow Z_{tot} = \frac{Rj\omega L}{R + j\omega L} = \frac{RpL}{R + pL} \text{ met } p = j\omega$$

② Spanningsdeeler: $V_2 = \frac{Z_{tot}}{9R + Z_{tot}} \cdot V_1$

$$\frac{V_2}{V_1} = \frac{R_{pL}}{R + pL} / 9R + \frac{R_{pL}}{R + pL}$$

$$= \frac{pL}{9R + 10pL}$$

$$= \frac{pL}{9R} \left(\frac{1}{1 + \frac{10pL}{9R}} \right)$$

$$p = j\omega = j2\pi f$$

$$= \frac{j2\pi fL}{9R} \left(\frac{1}{1 + \frac{20j\pi fL}{9R}} \right)$$

$$(*) = A \cdot j \frac{1}{f_c}$$

$$\Leftrightarrow A \cdot \frac{20\pi L}{9R} = \frac{2\pi L}{9R} \Rightarrow A = \frac{1}{10}$$

$$(*) \frac{1}{1 + j\frac{f}{f_c}} \Rightarrow f_c = \frac{9R}{20\pi L} = \frac{9}{10} \cdot \frac{R}{2\pi L} = 0,9 \text{ kHz}$$


$$\Rightarrow \frac{V_2}{V_1} = \frac{1}{10} \cdot \frac{j\frac{1}{f_c}}{1 + j\frac{f}{f_c}}$$

③ Amplitude transfer: $\left| \frac{V_2}{V_1} \right| = \frac{1}{10} \cdot \frac{j\frac{1}{f_c}}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$


$$f \ll f_c : \left| \frac{V_2}{V_1} \right| \approx \frac{1}{10} \cdot \frac{j\frac{1}{f_c}}{1} \Rightarrow \# \text{ dB} = \overset{+ \text{ dus}}{20 \log f} + 20 \log \frac{1}{10}$$

$$f = f_c : \left| \frac{V_2}{V_1} \right| = \frac{1}{10\sqrt{2}} \Rightarrow \# \text{ dB} = -23 \text{ dB}$$

$$f \gg f_c : \left| \frac{V_2}{V_1} \right| \approx \frac{1}{10} \Rightarrow \# \text{ dB} = 20 \log \frac{1}{10} = -20$$

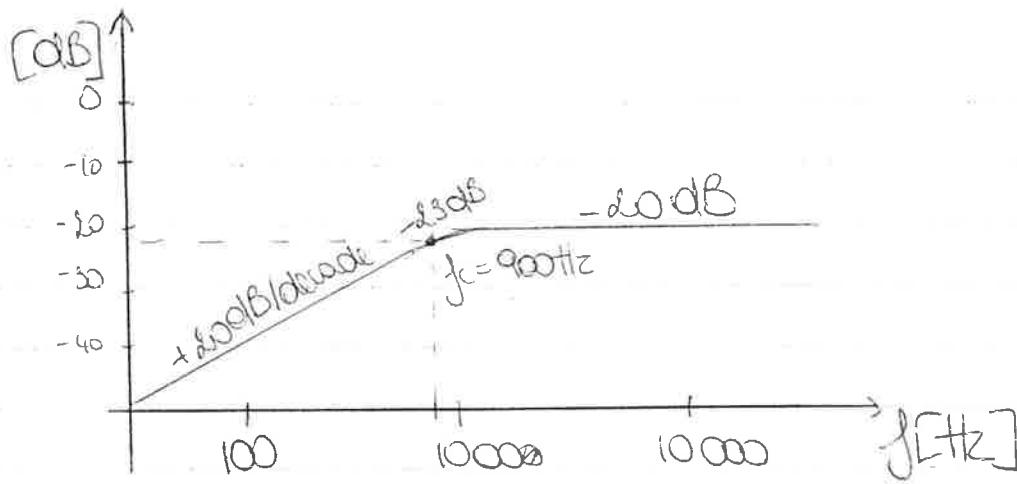

oef 3

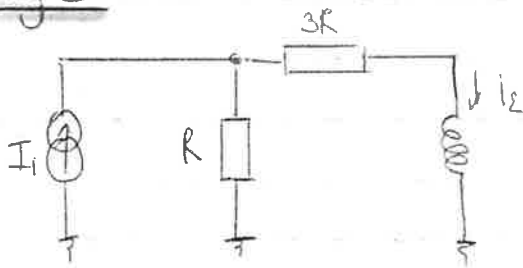

① $Z_R = 3R$ & $Z_L = j\omega L$ & serie
 $\Rightarrow Z_{tot} = 3R + j\omega L$

② Stromdeling: $I_2 = \frac{R}{R + Z_{tot}} \cdot I_1$

$$\frac{I_2}{I_1} = \frac{R}{R + 3R + j\omega L}$$

met $p = j\omega$
 $= j2\pi f$

hoe zet je seconden om
 in Hz? $\text{Hz} = \text{s}^{-1}$

dus $\frac{\pi L}{R} = 2 \text{ ms}$

$\Rightarrow \frac{R}{\pi L} = \frac{1}{2} \text{ kHz}$

$$= \frac{1}{4} \cdot \frac{1}{1 + \frac{j\omega L}{4R}}$$

$$= \frac{1}{4} \cdot \frac{1}{1 + \frac{j2\pi f L}{4R}}$$

$$= \frac{1}{4} \cdot \frac{1}{1 + j \frac{f}{f_c}}$$


met $f_c = \frac{2R}{\pi L} = 2 \cdot \frac{1}{2} \text{ kHz} = 1 \text{ kHz}$

$$\textcircled{3} \text{ Amplitude transfer} = \left| \frac{I_2}{I_1} \right| = \frac{1}{4} \cdot \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$


$$\text{+ } f \ll f_c : \left| \frac{I_2}{I_1} \right| \approx \frac{1}{4} \Rightarrow \# \text{ dB} = 20 \log \frac{1}{4} = -12 \text{ dB}$$

$$\text{+ } f = f_c : \left| \frac{I_2}{I_1} \right| = \frac{1}{4\sqrt{2}} \Rightarrow \# \text{ dB} = -15 \text{ dB}$$

$$\text{+ } f \gg f_c : \left| \frac{I_2}{I_1} \right| = \frac{1}{4} \cdot \frac{f_c}{f} \Rightarrow \# \text{ dB} = 20 \log f_c - 20 \log f + 20 \log \frac{1}{4}$$

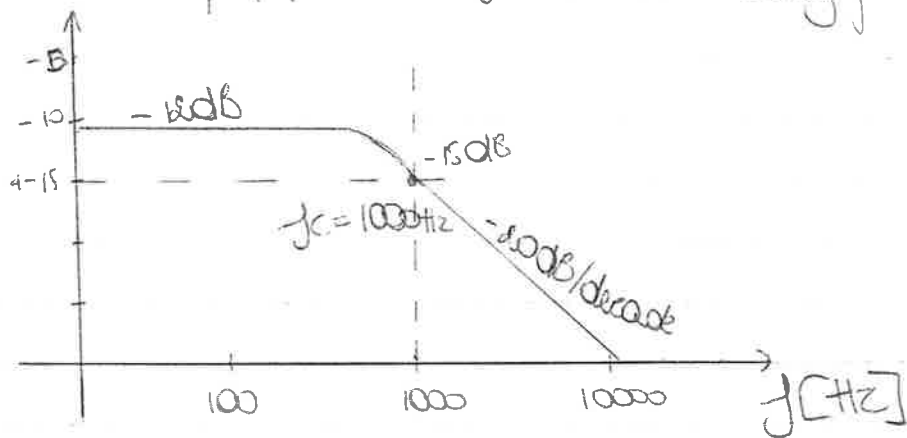

ex 4

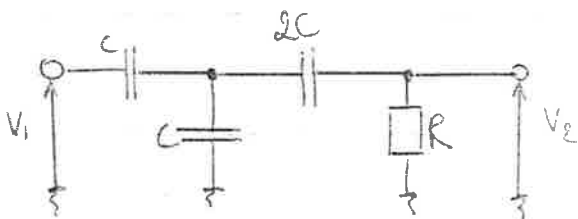

$$\pi RC = 100 \text{ ns}$$

$$\frac{1}{\pi RC} = \frac{1}{100 \cdot 10^{-9}} \text{ Hz} = 10 \text{ kHz}$$

$$\textcircled{1} Z_C = \frac{1}{j\omega C} \Rightarrow \frac{1}{Z_{tot}} = j\omega C + j\omega C = 2j\omega C \Rightarrow Z_{tot} = \frac{1}{2j\omega C}$$

$$\textcircled{2} \frac{1}{Z_{tot}} = 2j\omega C + 2j\omega C = 4j\omega C \Rightarrow Z_{tot} = \frac{1}{4j\omega C} = \frac{1}{4\omega C}$$


$$\textcircled{3} \text{ Spannungsteiler: } V_E = \frac{Z_{tot}}{R + Z_{tot}} \cdot V_i$$

$$\frac{V_E}{V_i} = \frac{\frac{1}{4\omega C}}{R + \frac{1}{4\omega C}}$$

$$= \frac{1}{1 + 4RC}$$

$$= \frac{1}{1 + 4RC f_{\text{eff}}}$$
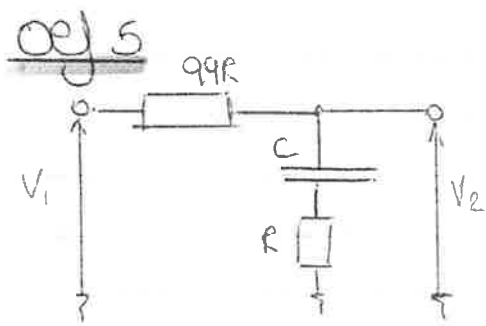
$$= \frac{1}{1 + \frac{f}{f_c}} \quad \text{met } f_c = \frac{1}{8\pi RC} =$$



$$\frac{1}{\pi RC} = \frac{1}{50 \cdot 10^{-6} \text{ s}} = 20 \text{ kHz}$$

① $Z_R = R$ & $Z_C = \frac{1}{j\omega C}$ & serie

$$\Rightarrow Z_{\text{tot}} = R + \frac{1}{j\omega C} = \frac{Rj\omega C + 1}{j\omega C} = \frac{R\omega C + 1}{\omega C}$$

met $p = j\omega = j2\pi f$

② Spannungsteiler: $V_2 = \frac{Z_{\text{tot}}}{99R + Z_{\text{tot}}} \cdot V_1$

$$\begin{aligned} \frac{V_2}{V_1} &= \frac{R\omega C + 1}{\omega C} / 99R + \frac{R\omega C + 1}{\omega C} \\ &= \frac{R\omega C + 1}{1 + 100R\omega C} \\ &= \frac{Rj2\pi f C + 1}{1 + 100Rj2\pi f C} \end{aligned}$$

* $1 + j\frac{f}{f_c}$ met $f_c = \frac{1}{R2\pi C} = 10 \text{ kHz}$

* $1 + j\frac{f}{f_{c1}}$ met $f_{c1} = \frac{1}{100R2\pi C} = 100 \text{ Hz}$

$$= \frac{1 + jf/f_c}{1 + jf/f_{c1}}$$

③ Amplitudentransfekt: $\left| \frac{V_2}{V_1} \right| = \frac{1 + jf/f_c}{\sqrt{1 + (jf/f_{c1})^2}}$


* $f \ll f_c$: $\left| \frac{V_2}{V_1} \right| \approx 1 \Rightarrow \# \text{ dB} = 20 \log 1 = 0 \text{ dB}$

$$\bullet f = f_{c2} : \left| \frac{V_2}{V_1} \right| = \frac{1}{\sqrt{2}} \Rightarrow \#dB = 20 \log \frac{1}{\sqrt{2}} = -3dB$$

$$\bullet f_{c1} < f < f_{c2} : \left| \frac{V_2}{V_1} \right| = \frac{f_{c2}}{f} \Rightarrow 20 \log f_{c2} - 20 \log f$$

$$\bullet f = f_{c1} : \left| \frac{V_2}{V_1} \right| = \frac{\sqrt{2}}{f_{c1}/f} \Rightarrow$$

ex 6

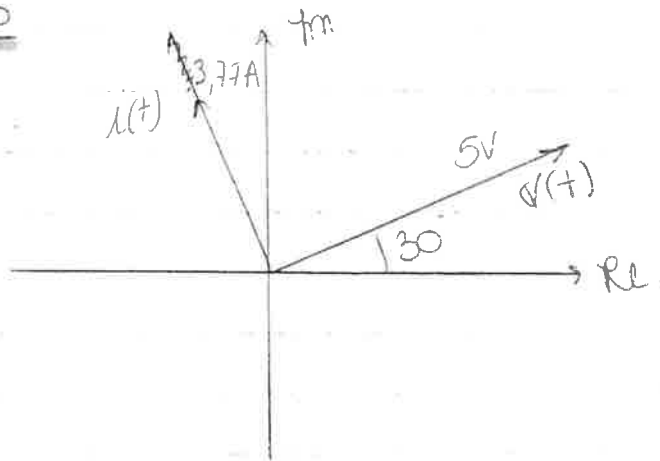

$+90^\circ \Rightarrow$
condensator


$$Z = \frac{5V}{3,77A} \cdot e^{j(-90^\circ)} = j \cdot \frac{5V}{3,77A}$$

$$Z_C = \frac{V_C}{I_C} = \frac{1}{j\omega C}$$

$$C = \frac{1}{j\omega Z_C} = \frac{3,77A}{j^2 \cdot 2\pi f \cdot 5V} = 20 \mu F$$

$$j^2 = -1$$

obj 7

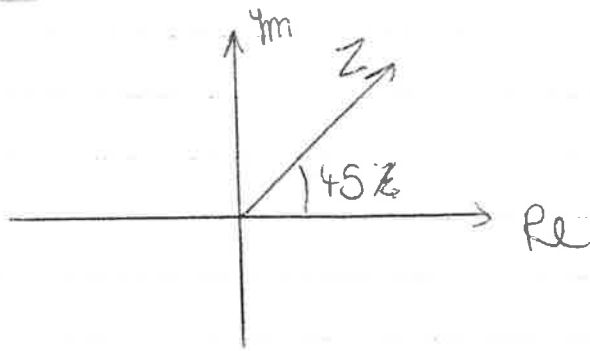

$$\begin{aligned} * Z &= \frac{V}{i} = \frac{28V \cdot e^{j68^\circ}}{9mA \cdot e^{j23^\circ}} = \frac{28V}{9mA} \cdot e^{j45^\circ} \\ &\quad \downarrow \cos 45^\circ = \frac{\sqrt{2}}{2} \\ &= \frac{28V}{9mA} \cdot \frac{\sqrt{2}}{2} + j \cdot \frac{28V}{9mA} \cdot \frac{\sqrt{2}}{2} \\ &= R + L \end{aligned}$$


$$Z = 2,2k\Omega \cdot (1 + j)$$

$$\begin{aligned} * j2\pi f_1 \cdot L &= j \cdot \frac{28V}{9mA} \cdot \frac{\sqrt{2}}{2} \\ \Rightarrow L &= 70\mu H \end{aligned}$$

$$* R = \frac{V}{I} \cdot \frac{\sqrt{2}}{2} = \frac{28V}{9mA} \cdot \frac{\sqrt{2}}{2} = 2,2k\Omega$$

Oefeningen H7

oef 1

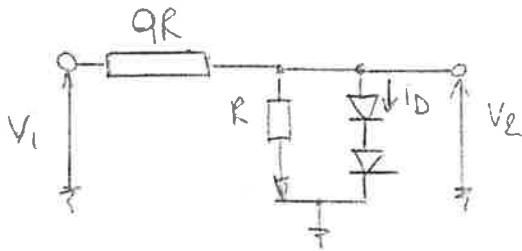

Diodes zijn in serie $\Rightarrow$ $\begin{cases} \text{ze geleiden} \\ \text{ze sperren} \Rightarrow I = 0 \end{cases}$


a) geleiden: I_D moet pos zijn

$$V_2 = 0,7V + 0,7V = 1,4V$$

$$I_D = \frac{V_1 - 1,4V}{9R} - \frac{1,4V}{R} > 0$$

$$\begin{aligned} I_D &= I_{tot} - I_R \\ &= \frac{V_{ge}}{9R} - \frac{V_R}{R} \\ &= \frac{V_1 - 1,4V}{9R} - \frac{1,4V}{R} \end{aligned}$$
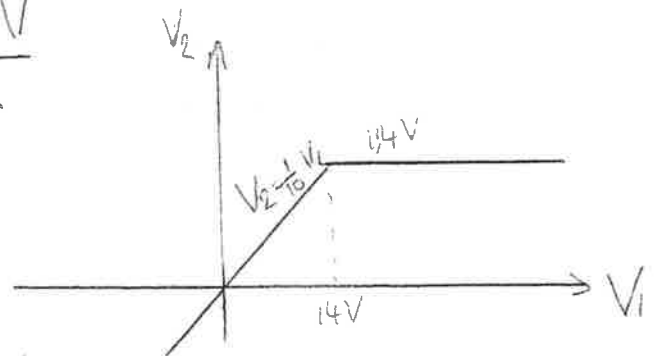
$$\begin{aligned} V_2 &= 1,4V \\ V_1 &\geq 14V \end{aligned}$$



b) sperren: $V_D < 0,7V$

$$V_2 = \frac{1}{10} V_1$$

$$V_1 < 14V \Rightarrow V_2 = \frac{1}{10} V_1$$

af 3

1) beide geleiden:

$$V_1 - V_{R_1} - V_{D_1} - V_{D_2} = 0$$

$$V_1 - V_{R_1} = V_{D_1} + V_{D_2} = 1,4V$$

$$V_1 - 1,4V = I_1 \cdot R_1$$

$$I_1 = \frac{V_1 - 1,4V}{R_1}$$

$$\Rightarrow \frac{V_1 - 1,4V}{R_1} > 0$$

$$V_1 > 1,4V$$

$$\Rightarrow I_1 - \frac{0,7V}{R} - I_2 = 0$$

$$\Rightarrow I_2 = \frac{V_1 - 1,4V - 0,7V}{R}$$

$$V_1 > 2,1V$$

2) ~~D₁~~ geleitet, D₂ sperrt.

$$V_1 - V_{R_1} - V_{D_1} - V_{R_2} = 0$$

$$V_1 - V_{R_1} - V_{R_2} = 0,7V$$

$$V_1 - 0,7V = 2R \cdot I_1$$

$$I_1 = \frac{V_1 - 0,7V}{R_1} > 0$$

$$\Rightarrow V_1 > 0,7V$$

3) beide sperren: $I_1 = I_2 = 0$

$$\Rightarrow V_1 < 0,7V$$

Def 4

a) geilen.

$$V_L = 2,1V$$

$$2,1V - V_R - 0,7V = 0$$

$$1,4V = V_R$$

$$1,4V = R_1(I - I_D)$$

$$R_1 I_D = R_1 I - 1,4V$$

$$I_D = R_1 I - \frac{1,4V}{R}$$

$$I_D > 0$$

$$I > \frac{1,4V}{R}$$

b) D_1 geilen, rest spert

$$V_L = V_R + 0,7V$$

$$V_L = I_R R + 0,7V$$

$$V_L = V_{R1} + V_{R2}$$

$$0,7V + I_1 R = I_D R + R(I - I_D)$$

$$I_D = I_1 - \frac{0,7V}{R}$$

$$I_D > 0 \Rightarrow I_1 > \frac{0,7V}{R}$$

c) ~~alternativ~~

$$V_L = 2R \cdot I_D$$


$$I_D < \frac{0,7V}{R}$$

oef 5

$$V_{BE} = 0,7V$$

$$I_C = \beta \cdot I_B$$

+ wet v. Ohm en Kirchhoff

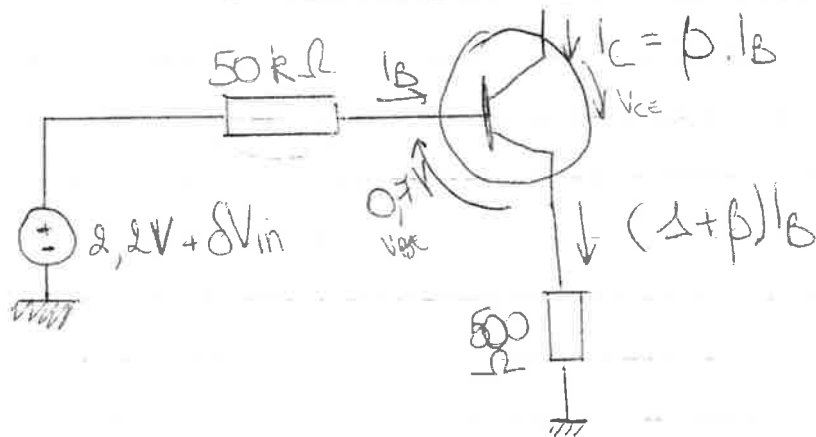

Oplossing 1) $2,2V + \delta V_{in} = 50k\Omega \cdot I_B + 0,7V + 500\Omega \cdot 200 \cdot I_B$

$$\Rightarrow I_B = 10nA + \frac{\delta V_{in}}{150k\Omega}$$

$$2) I_C = \beta \cdot I_B$$

$$= 2mA + \frac{4}{3} \frac{\delta V_{in}}{k\Omega}$$

$$\begin{aligned} 3) V_{out} &= 12V - 3k\Omega \cdot I_C \\ &= 12V - 6V - 4\delta V_{in} \\ &= 6V - 4\delta V_{in} \end{aligned}$$

↳ versterker v/d ingangsspanning
polariteitsinversie

stijgende input V $\Rightarrow$ dalende V_{out}

oef 6

3 werkingsgebieden die complementaire zijn.
 V_E i/v V_I voor $0 \leq V_I \leq 5V$

oef.

3 gebieden $\begin{cases} \nearrow \text{cut-off} \\ \rightarrow \text{lineaire} \\ \searrow \text{saturatie} \end{cases}$

cut-off	$V_{BE} < 0,7V$
lineaire	$V_{BE} = 0,7V$
	$I_C = \beta \cdot I_B$
	$V_{CE} > 0$
saturatie	$V_{BE} = 0,7V$
	$V_{CE} = 0V$
	$I_C < \beta \cdot I_B$

① cut-off (transistor geleidt niet)

$$I_B = I_C = I_E = 0A$$
$$V_{BE} < 0,7V$$

→ geen stroom → qn spanningval

$$V_E = 12V ; V_I < 0,7V$$

② lineaire : $V_{BE} = 0,7V$
 $V_{CE} > 0$
 $I_C = \beta \cdot I_B$

$$I_E = \frac{V_I - 0,7V}{100\Omega} \cong I_C$$

$$V_E = 12V - 500\Omega \cdot \frac{V_I - 0,7V}{100\Omega}$$
$$= 15,5V - 5V_I$$

$$\begin{aligned} 15,5V - 5V_1 &> V_1 - 0,7V \\ \Rightarrow 6V_1 &< 16,2V \\ V_1 &< 2,7V \end{aligned}$$

③ Saturatie : transistor geleidt

$$\begin{aligned} V_{BE} &= 0,7V \\ V_{CE} &= 0V \\ I_C &< \beta \cdot I_B \end{aligned}$$

$$\begin{aligned} V_2 &= V_1 - 0,7V \\ V_1 &> 2,7V \end{aligned}$$

oef 7

$$\begin{aligned} + I_B : 2,7V + \delta V_{in} &= V_{BE} + 600\Omega \cdot 200 \cdot I_B \\ &= 0,7V + 120000 I_B \end{aligned}$$

$$\Rightarrow I_B = \frac{1,0V}{60k\Omega} + \frac{\delta V_{in}}{120k\Omega}$$

$$\begin{aligned} + I_C = \beta \cdot I_B &= 200 \cdot \left(\frac{1,0V}{60k\Omega} + \frac{\delta V_{in}}{120k\Omega} \right) \\ &= \frac{10}{3} \text{ mA} + \frac{5}{3} \frac{\delta V_{in}}{k\Omega} \end{aligned}$$

$$\begin{aligned} + V_{out} &= 20V - 2k\Omega I_C - 3k\Omega I_C \rightarrow \text{parallel?} \\ &= 20V - \frac{20V}{3} - \frac{10}{3} \delta V_{in} = 10V - 5\delta V_{in} \end{aligned}$$

$$R_{id} = \frac{6}{5}$$

Extra op

$$\begin{aligned} * I_B: 2,1V + \delta V_{in} &= 7k\Omega \cdot I_B + V_{BE} * \\ &= 7k\Omega \cdot I_B + 0,7V \end{aligned}$$

$$\begin{aligned} \Rightarrow I_B &= \frac{1,4V}{7k\Omega} + \frac{\delta V_{in}}{7k\Omega} \\ &= 0,2mA + \frac{1}{7} \frac{\delta V_{in}}{k\Omega} \end{aligned}$$

$$\begin{aligned} * I_C &= 100 \cdot \left(0,2mA + \frac{1}{7} \frac{\delta V_{in}}{k\Omega} \right) \\ &= \cancel{200mA} + \frac{100}{700} \frac{\delta V_{in}}{k\Omega} \\ &= 0,2A \end{aligned}$$

$$\begin{aligned} * V_{out} &= 24V - 700\Omega \cdot I_C - 700\Omega \cdot I_C \\ &= 24V - 140V - 10000 \delta V_{in} - 140V \end{aligned}$$

$$\begin{aligned} \frac{1}{R_{tot}} &= \frac{1}{700} + \frac{1}{700} = \frac{2}{700} \\ \Rightarrow R_{tot} &= 350\Omega \end{aligned}$$

$$\begin{aligned} V_{out} &= 24V - 350\Omega I_C \\ &= 24V - 350\Omega \left(\frac{200mA}{0,02A} + \frac{1}{70} \frac{\delta V_{in}}{k\Omega} \right) \\ &= 24V - 7V - 5\delta V_{in} \end{aligned}$$

oefeningen H8

oef 1

$$\begin{aligned} Z &= \bar{A} \cdot \bar{B} \cdot \bar{C} + BCD + (\bar{B}\bar{C} + A\bar{B}) \cdot (\bar{B}\bar{C} + CD) + BC\bar{D} + A(\bar{C} + BD) \\ &= \bar{A} \cdot \bar{B} \cdot \bar{C} + BCD + \bar{B}\bar{C} + A\bar{B} \cdot CD + BC\bar{D} + A\bar{C} + ABD \\ &= \bar{A} \cdot \bar{B} \cdot \bar{C} + BC(D + \bar{D}) + \bar{B}\bar{C} + A\bar{B}CD + A\bar{C} + ABD \\ &= \bar{A} \cdot \bar{B} \cdot \bar{C} + B(C + \bar{C}) + A\bar{B}CD + A\bar{C} + ABD \\ &= \bar{A} \cdot \bar{B} \cdot \bar{C} + B + A\bar{B}CD + A\bar{C} + ABD \\ &= \bar{C}(\bar{B}\bar{A} + A) + B + A\bar{B}CD + ABD \\ &= \bar{C}(A + \bar{B}) + B + AD(\bar{B}C + B) \\ &= \bar{C}(A + \bar{B}) + B + AD(B + C) \\ &= A\bar{C} + C\bar{B} + B + ADB + ADC \\ &= \bar{C} + B + A(\bar{C} + DC) + ADB \\ &= B + \bar{C} + A(\bar{C} + D) + ADB \\ &= B + \bar{C} + A\bar{C} + AD + ADB \\ &= \cancel{B + AD} + \\ &= B + \bar{C}(A + 1) + AD(B + 1) \\ &= B + \bar{C} + AD \end{aligned}$$

oef 2

$$Z = \underbrace{(\bar{A}\bar{B} + \overline{(\bar{A}\bar{B}D + \bar{A}C)})}_{\textcircled{1}} \cdot \underbrace{((\bar{B}\bar{C}) \cdot (A + C))}_{\textcircled{2}}$$

$$\begin{aligned} \textcircled{1} \quad \bar{A}\bar{B} \cdot \overline{(\bar{A}\bar{B}D + \bar{A}C)} &= (\bar{A} + B) \cdot (\bar{A}\bar{B}D + \bar{A}C) \\ &= \bar{A}C + \bar{A}BC \\ &= \bar{A}C(B + 1) \\ &= \bar{A}C \end{aligned}$$

$$\textcircled{2} \quad \bar{B}\bar{C} + \overline{(A + C)} = \bar{B}\bar{C} + \bar{A} \cdot \bar{C}$$

$$\Rightarrow Z = \bar{A}C \cdot (\bar{B}\bar{C} + \bar{A}\bar{C}) = \bar{A}BC$$

$$A + \bar{A}B = A + B$$

ex 3

$$\begin{aligned}
 Z &= \bar{A} \cdot \bar{C} + (\bar{C} + A) \cdot (\bar{B} + \bar{D}) + (A \cdot (D + B \cdot \bar{C})) \\
 &= \bar{A} \cdot \bar{C} + (\bar{C} + A) + (\bar{B} + \bar{D}) + (AD + AB\bar{C}) \\
 &= \bar{A} \cdot \bar{C} + \bar{A}C + B \cdot D + AD + AB\bar{C} \\
 &= \bar{A} + BD + AD + AB\bar{C} \\
 &= \bar{A} + D(B + A) + AB\bar{C} \\
 &= (\bar{A} + AB\bar{C}) + AD + BD \\
 &= \boxed{\bar{A}} + B\bar{C} + \boxed{AD} + DD \\
 &= \bar{A} + \cancel{D} + B\bar{C} + \cancel{D}D \\
 &= \bar{A} + B\bar{C} + D(B + 1) \\
 &= \bar{A} + D + B\bar{C}
 \end{aligned}$$

ex 4

$$\begin{aligned}
 Z &= \bar{B} + \bar{A} + \bar{A} \cdot C \cdot D \\
 &= \bar{A}(\bar{B} + CD) \\
 &= \bar{A}(\bar{B} + CD) \\
 &= \bar{A} \cdot (\bar{B} + CD) \\
 &= \bar{A} \cdot (B \cdot \overline{CD})
 \end{aligned}$$

of 5

$$D_0 = \overline{Q_0}$$

$$D_1 = Q_0 \cdot Q_1 + Q_0 \cdot \bar{Q}_2 \cdot \bar{Q}_1$$

$$D_2 = Q_1 \cdot Q_0 + Q_2 \bar{Q}_0$$

CK	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
Q_0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
Q_1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0
Q_2	0	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
$(Q_2 Q_1 Q_0)_2$	0	1	2	3	4	5	0	1	2	3	4	5	0	1	2	3	4	5

periodische Perikard

Def 6 $\rightarrow$ nicht kurren.

$$D_0 = \overline{Q_0}$$

$$Q_1 = \overline{Q_1} \cdot \overline{Q_2}$$

$$D_2 = Q_1$$

CK				
Q_0	0	1	0	1
Q_1	0	0	1	
Q_2	0	0	0	1
$(Q_2 Q_1 Q_0)_2$	0	1	2	

ex 8

$$N_1 =$$

$$N_2 =$$

$$N_3 =$$

$$N_4 =$$

$$N_5 = \frac{1}{800ns} \cdot 4096 =$$

Entree oef #8

oef 1

$$\begin{aligned} Z &= (\bar{A}E + (\overline{A \cdot \bar{A}B})) \cdot (\bar{A}C + \bar{C} + \bar{C}\bar{E}) \cdot (\bar{A}\bar{D}) \rightarrow \text{opsplitsen in} \\ &= (\bar{A}E + (\bar{A} + AB)) \cdot (\bar{A}C + \bar{C} + \bar{C}\bar{E}) \cdot (\bar{A} + D) \quad \text{3 werken} \\ &= (\bar{A}E + \bar{A} + AB) (\bar{A}C + \bar{C}(\bar{E} + 1)) (\bar{A} + D) \quad \text{makkelijker} \\ &= (\bar{A}(E + 1) + AB) (\bar{A}C + \bar{C}) (\bar{A} + D) \\ &= (\bar{A} + D) (\bar{C} + \bar{A}) (\bar{A} + D) \\ &= (\bar{A} + D) (\bar{A}\bar{C} + \bar{A} + \bar{C}D + \bar{A}D) \\ &= (\bar{A} + D) (\bar{A}(\bar{C} + 1) + \bar{C}D + \bar{A}D) \\ &= (\bar{A} + D) (\bar{A} + \bar{C}D) \\ &= \bar{A} + \bar{A}\bar{C}D + \bar{A}D + D\bar{C}D \\ &= \bar{A} + \bar{C}D \\ &= \bar{A}(D + 1) + \bar{C}D(\bar{A} + D) + D\bar{C}D \\ &= \bar{A} + \bar{A}\bar{C}D + D\bar{C}D \\ &= \bar{A} + D\bar{C}D \end{aligned}$$

oef 1

$$\begin{aligned} D_0 &= \bar{Q}_0 \bar{Q}_1 + (Q_1 \oplus Q_2) \\ D_1 &= \bar{Q}_0 + Q_2 \\ D_2 &= Q_1 \end{aligned}$$

Extra 02 H8

021

$$Z = (\bar{A}E + \overline{(A \cdot (\bar{A}B))}) \cdot (\bar{A}C + \bar{C} + \bar{C}\bar{E}) (\bar{A}D)$$

$$\begin{aligned} \textcircled{1} &= \bar{A}E + \bar{A} + AB \\ &= \bar{A}(E+1) + AB \\ &= \bar{A} + AB \\ &= \bar{A} + B \end{aligned}$$

$$\begin{aligned} \textcircled{2} &= \bar{A}C + \bar{C}(E+1) \\ &= \bar{A}C + \bar{C} \\ &= \bar{C} + \bar{A} \end{aligned}$$

$$\textcircled{3} = \bar{A} + D$$

$$\begin{aligned} \Rightarrow & (\bar{A} + B)(\bar{C} + \bar{A})(\bar{A} + D) \\ &= \bar{A}\bar{C} + \bar{A} + \bar{A}B\bar{C} + B\bar{A} + \bar{A}CD + \bar{A}D + B\bar{C}D + \bar{A}BD \\ &= \bar{A}(C+1) + \bar{A}B(C+1) + \bar{A}D(\bar{C}+1) + B\bar{C}D + \bar{A}BD \\ &= \bar{A}(B+1) + \bar{A}D + B\bar{C}D + \bar{A}BD \\ &= \bar{A} + B\bar{C}D + \bar{A}BD \\ &= \bar{A} + B\bar{C}D \end{aligned}$$

ay 1

$$D_0 = \bar{Q}_0 + Q_2 \quad \bar{Q}_1 + (Q_1 \oplus Q_2)$$

$$D_1 = \bar{Q}_0 + Q_2$$

$$D_2 = \bar{Q}_1 + (\bar{Q}_0 + Q_2)$$

	ck					
Q_0		0	1	1	1	0
Q_1		1	1	0	1	1
Q_2		0	0	1	1	0
$(Q_2 Q_1 Q_0)_2$		2	3	5	7	2

periodik tekrard